

# UP-TO-DATE INVENTION

## The RotoVerter from arkresearch



*Editor's: The description of this invention was received from Hector D. Perez Torrez, designer of the "RV" Rotoverter and TV transverter OU "transformation" devices.*

Here is the first prototype, used to test a 3PH generator. Light bulb was a 100W 120V, AC generator required 380W for excitation to 120VAC plus the light bulb load for a total of 480W. Input to rotoverter was 240W for a total of 200% efficiency from the prime mover. Friction loss and prime mover loss was not calculated, PF unity, 120VAC unto a purely resistive load excitation pure DC120VDC3.1666667A (380W) + 100W = 480W. - 240W=240 excess.

It is a common 3PH dual winding 230/460V motor wired to 480V run at 120v as a ROTOPHASE converter. That's the beauty of it, OFF the shelf components preferably totally enclosed motors (so fan can be removed) low friction bearings, from 3HP to 7.5HP. Re-rating hp can be from 1/7 to 1/3 the original HP (some motors can run up to 1/2 HP capacity but will require extreme care and cooling.... and exact tuning to load).

System requires starting and running capacitance; the perfect starting capacitance is the one that gives same plate current value as 480V but running at 120V. The best running capacitance is the one that gives the lowest Amperage reading at programmed load. (ALL capacitors are AC 370V OIL "no electrolytic").

Some motors are better than others; also for generator use you must choose the over-unity generator and motor combination to obtain OU. It looks easy to gain it, but requires quite a good choice of items and common sense. In this Research we have found even a few turns or a run weld in stator can change drastically the results. Up to date best performance has being obtained from US (motors 7.5 HP, BALDOR 3,5, HP, GE 3HP totally enclosed, dual winding 230/460V). Higher HP will require professional expertise in industrial electricity and power eng. (not recommended for amateur experimenter). Anyone engaged in this experiments must be familiar with safety procedures and basic electric and mechanic knowledge. Voltages and rotating machinery must be handled with great care. SEE basic diagram and connection.

### 9 Lead 3HP Wye-Connected Motor

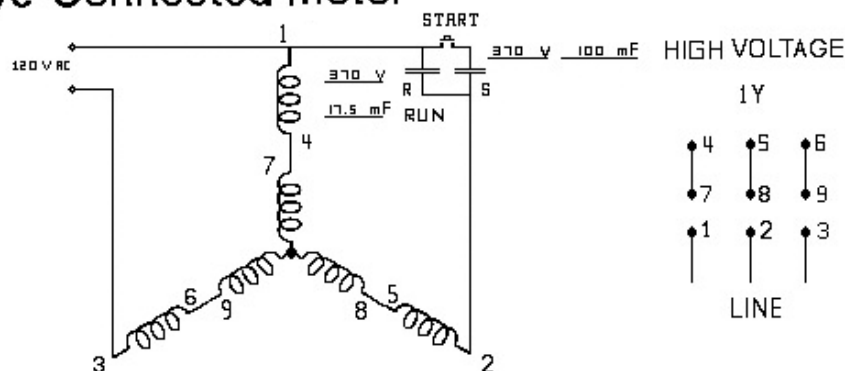


Fig. 1


**Latest UPDATE BELOW 7-01-02**

ARK RESEARCH

2002

```
Starting current > 9.0 A
running voltage 120.0 V
running current  3.00 A
                PT 360.0 W
```
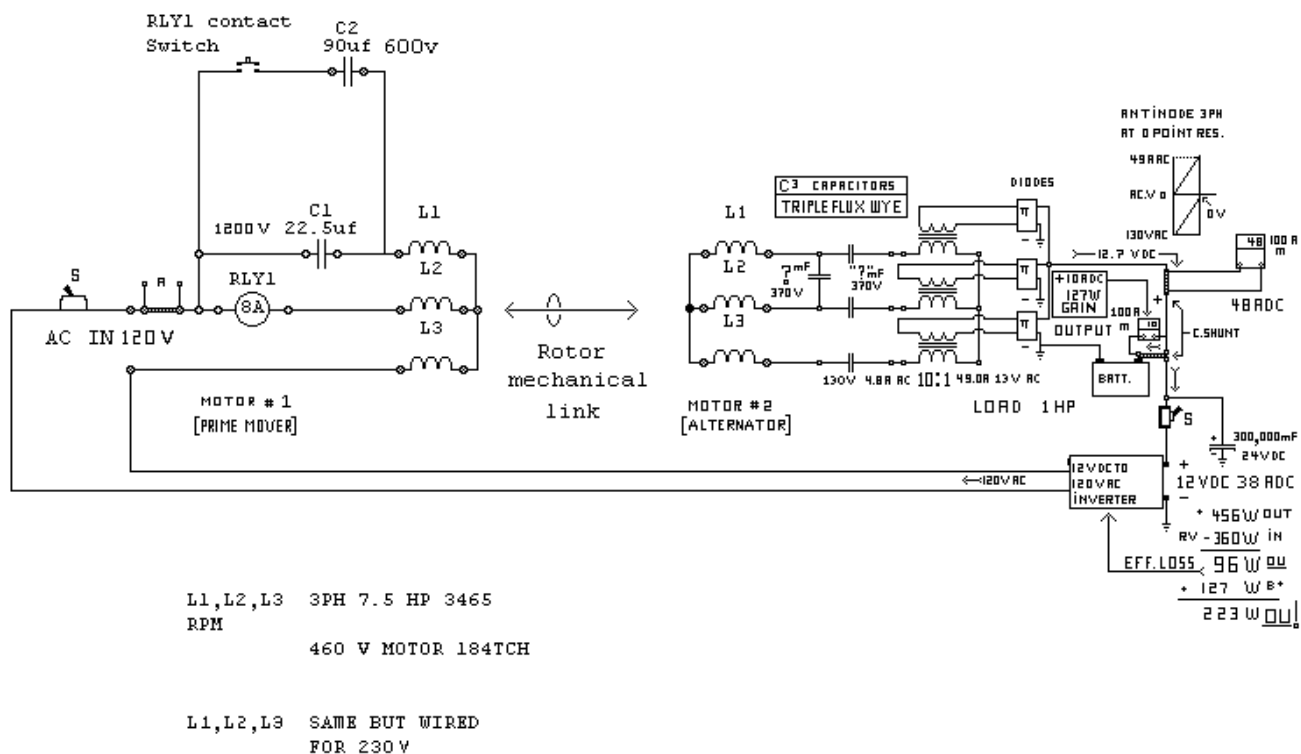
## EXPERIMENT ON MAGNETIC ROTO AMPLIFICATION



THERMAL & MECHANICAL LOSS WAS NOT CALCULATED

Fig.2

**Subject: RV Basic level 1 Full MODEL Disclosure (Public domain)**

This is the RV (Level 1) plan of a full looped RV system:

Battery provides primary power for 12VDC to 120VAC. As to run prime mover (Roto-converter), second motor acts as an squirrel cage self-excited generator, a triple flux-capacitor LC tank tuned to best Standing wave condition as to create standing wave current node internally in battery at 0 voltage to battery "negative resistor". At 0 volts "voltage" a negative current is created as to maintain a reverse flow (charge) to battery exceeding the forward drain of the inverter demand, detuning system with a forward charge at 10 amperes with a voltage rise of approximately 0.83333 V over the battery. Voltage charge produces OU transform from the 0 point standing wave component. System gains energy from stochastic resonance within the LC tank components draining energy from "thermal" signature of the Aether and K thermodynamic-thermoelectric ambient heat (Electron spin). This is a full disclosure of an operational and tested device. System is made of standard off shelf items. Tuning is made by changing capacitor values and the proper selection of standard items for its construction, 3PH motors, 10:1 12V or 5:1 24V transformers with the proper core and winding values (standard) off shelf, diode bridges capacitor (all standard).

**Warning:** System opens (NON standard) space-time anomaly as time is reversed due to aether energy transform....

**Extreme warning:** Do not exceed 10KW Nor use of trans-uranic elements near unit as they may reach critical mass by regressive "inversed" decay. PB 206, U235, U238 must be maintained as far as possible from unit.

**Extreme Warning:** Dangerous Toy, Eldridge, Event horizon and hell raiser effects may be created by protoplasmic fields at extreme potentials PK.

Use wisely. You Can create Paradise or open the gates to Armageddon.

The choice is yours now....

Hector D Perez Torrez